

A generating set for the class of series-parallel minimally reactive bicubic impedances

Timothy H. Hughes (thh22@cam.ac.uk)

Workshop on Networks and Control, Wednesday 5th July 2017


Cambridge University Engineering Department

Motivation (courtesy of Malcolm)

Passive Network Synthesis Revisited

Malcolm C. Smith

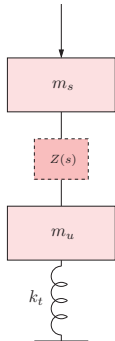THE MOST GENERAL PASSIVE VEHICLE SUSPENSION









Replace the spring and damper with a general positive-real impedance $Z(s)$.

But is $Z(s)$ physically realisable?

MTNS 2006, Kyoto, 24 July, 2006

Navigation icons: back, forward, search, and other presentation controls.

Motivation (courtesy of Malcolm)

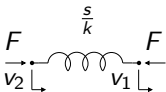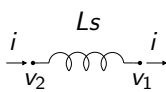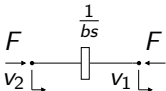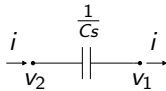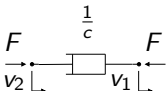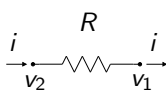Mechanical	Electrical
 $\frac{dF}{dt} = k(v_2 - v_1)$ $k > 0$ <p>spring</p>	 $\frac{di}{dt} = \frac{1}{L}(v_2 - v_1)$ $L > 0$ <p>inductor</p>
 $F = b \frac{d(v_2 - v_1)}{dt}$ $b > 0$ <p>inerter</p>	 $i = C \frac{d(v_2 - v_1)}{dt}$ $C > 0$ <p>capacitor</p>
 $F = c(v_2 - v_1)$ $c > 0$ <p>damper</p>	 $i = \frac{1}{R}(v_2 - v_1)$ $R > 0$ <p>resistor</p>

Minimal realisations

MINIMAL: least possible number of elements

MINIMALLY REACTIVE: impedance degree = no. reactive elements

Minimal and minimally reactive

Degree	Series-parallel	General
Bilinear		
Biquadratic		

Minimal realisations

MINIMAL: least possible number of elements

MINIMALLY REACTIVE: impedance degree = no. reactive elements

Minimal and minimally reactive

Degree	Series-parallel	General
Bilinear	Cauer and Foster forms	
Biquadratic		

Minimal realisations

MINIMAL: least possible number of elements

MINIMALLY REACTIVE: impedance degree = no. reactive elements

Minimal and minimally reactive

Degree	Series-parallel	General
Bilinear	Cauer and Foster forms	
Biquadratic	Lin Jiang & Smith	

Minimal realisations

MINIMAL: least possible number of elements

MINIMALLY REACTIVE: impedance degree = no. reactive elements

Minimal and minimally reactive

Degree	Series-parallel	General
Bilinear	Cauer and Foster forms	
Biquadratic	Lin Jiang & Smith	Reichert Chen & Smith + Zhang, Jiang & Smith

Minimal realisations

MINIMAL: least possible number of elements

MINIMALLY REACTIVE: impedance degree = no. reactive elements

Minimal and minimally reactive

Degree	Series-parallel	General
Bilinear	Cauer and Foster forms	
Biquadratic	Lin Jiang & Smith	Reichert Chen & Smith + Zhang, Jiang & Smith

BUT minimal realisations need not be minimally reactive (Hughes & Smith + Hughes)

Minimal realisations

MINIMAL: least possible number of elements

MINIMALLY REACTIVE: impedance degree = no. reactive elements

Minimal and minimally reactive


Degree	Series-parallel	General
Bilinear	Cauer and Foster forms	
Biquadratic	Lin Jiang & Smith	Reichert Chen & Smith + Zhang, Jiang & Smith

BUT minimal realisations need not be minimally reactive (Hughes & Smith + Hughes)

CONJECTURE: minimal and minimally reactive realisations of the impedance $\frac{p_n s^n + p_{n-1} s^{n-1} + \dots + p_0}{q_n s^n + q_{n-1} s^{n-1} + \dots + q_0}$ (degree n) contain (at most) $n+1$ resistors




A (very) useful result

The Zobel/Norton transformation:

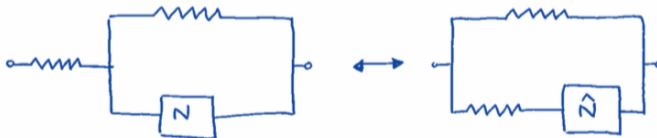


A (very) useful result



The Zobel/Norton transformation:

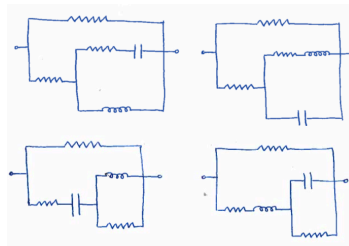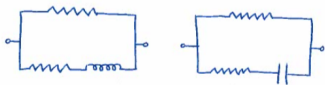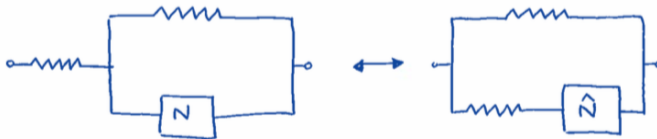







A (nonminimal) generating set

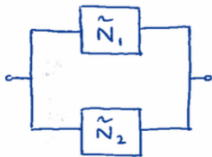


A (nonminimal) generating set

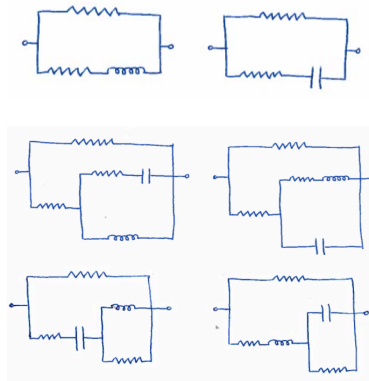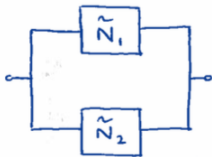

A (nonminimal) generating set

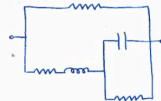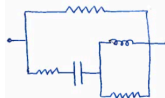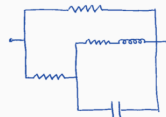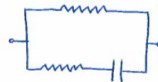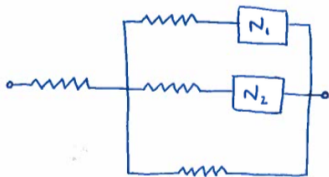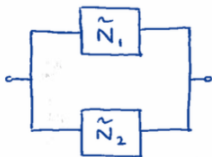


A minimal generating set


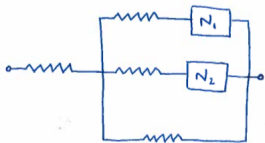


- 3 inductors or 3 capacitors: SOLVED
- Consider 2 inductors + 1 capacitor
- 1 inductor + 2 capacitor by *freq. inversion*
- other cases by duality


A minimal generating set

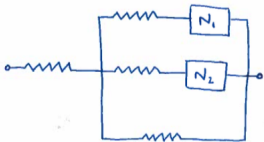

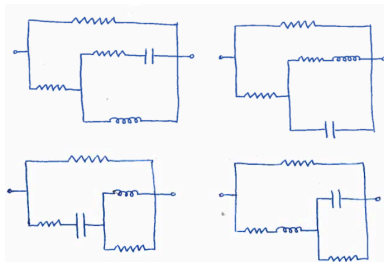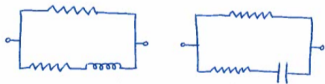- 3 inductors or 3 capacitors: SOLVED
- Consider 2 inductors + 1 capacitor
- 1 inductor + 2 capacitor by *freq. inversion*
- other cases by duality




A minimal generating set

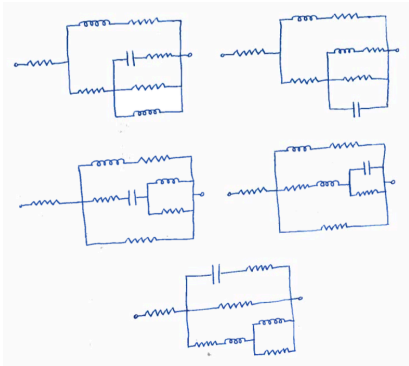


- 5 networks with 3 reactive elements and (at most) 5 resistors

A minimal generating set

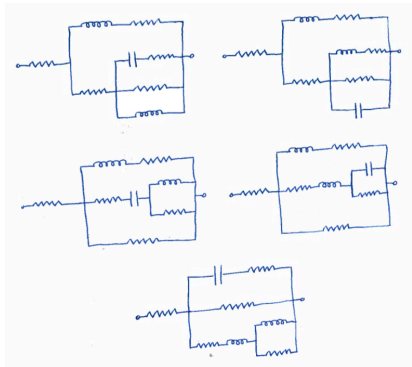

- 5 networks with 3 reactive elements and (at most) 5 resistors
- Set each of the series resistances/ parallel conductances to zero in turn:
- 25 networks with 3 reactive elements and 4 resistors (some duplicates)

A minimal generating set

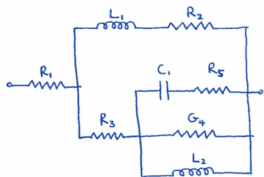


$$Z(s) = \frac{a(s)}{b(s)} = \frac{a_3 s^3 + a_2 s^2 + a_1 s + a_0}{b_3 s^3 + b_2 s^2 + b_1 s + b_0}$$

$$R_1 = \frac{\hat{a}}{\hat{b}}, \quad R_2 = \frac{\gamma_1 x}{\hat{b}^2}, \quad R_3 = \frac{\gamma_1 c_0}{\hat{b} d_0}, \quad G_4 = \frac{\hat{b} d_0 \gamma_7}{\gamma_4^2 \gamma_1},$$

$$R_5 = \frac{-\gamma_4^2 \gamma_3}{\hat{b}^3 d_0^2 S}, \quad L_1 = \frac{\gamma_1}{\hat{b}^2}, \quad L_2 = \frac{-\gamma_4 \gamma_1}{\hat{b} d_0^2}, \quad C_1 = \frac{-\hat{b}^3 d_0^2 S}{\gamma_4^3}$$

A minimal generating set

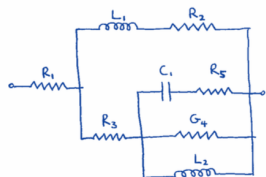

$$Z(s) = \frac{a(s)}{b(s)} = \frac{a_3 s^3 + a_2 s^2 + a_1 s + a_0}{b_3 s^3 + b_2 s^2 + b_1 s + b_0}$$

$$R_1 = \frac{\hat{a}}{\hat{b}}, \quad R_2 = \frac{\gamma_1 x}{\hat{b}^2}, \quad R_3 = \frac{\gamma_1 c_0}{\hat{b} d_0}, \quad G_4 = \frac{\hat{b} d_0 \gamma_7}{\gamma_4^2 \gamma_1},$$

$$R_5 = \frac{-\gamma_4^2 \gamma_3}{\hat{b}^3 d_0^2 S}, \quad L_1 = \frac{\gamma_1}{\hat{b}^2}, \quad L_2 = \frac{-\gamma_4 \gamma_1}{\hat{b} d_0^2}, \quad C_1 = \frac{-\hat{b}^3 d_0^2 S}{\gamma_4^3}$$


$$\hat{a}(x) = a(-x), \quad \hat{b}(x) = b(-x), \quad \gamma_1 = \hat{a} \frac{d\hat{b}}{dx} - \hat{b} \frac{d\hat{a}}{dx}$$

$$S = \begin{vmatrix} b_3 & b_2 & b_1 & b_0 & 0 & 0 \\ a_3 & a_2 & a_1 & a_0 & 0 & 0 \\ 0 & b_3 & b_2 & b_1 & b_0 & 0 \\ 0 & a_3 & a_2 & a_1 & a_0 & 0 \\ 0 & 0 & b_3 & b_2 & b_1 & b_0 \\ 0 & 0 & a_3 & a_2 & a_1 & a_0 \end{vmatrix}, \quad d_2 = \begin{vmatrix} 0 & 1 & 2x & x^2 & 0 \\ 0 & 0 & 1 & 2x & x^2 \\ b_3 & b_2 & b_1 & b_0 & 0 \\ 0 & a_3 & a_2 & a_1 & a_0 \\ 0 & b_3 & b_2 & b_1 & b_0 \end{vmatrix}, \quad d_1 = - \begin{vmatrix} 1 & 2x & x^2 & 0 & 0 \\ 0 & 0 & 1 & 2x & x^2 \\ b_3 & b_2 & b_1 & b_0 & 0 \\ 0 & a_3 & a_2 & a_1 & a_0 \\ 0 & b_3 & b_2 & b_1 & b_0 \end{vmatrix}, \quad d_0 = \begin{vmatrix} 1 & 2x & x^2 & 0 & 0 \\ 0 & 1 & 2x & x^2 & 0 \\ b_3 & b_2 & b_1 & b_0 & 0 \\ 0 & a_3 & a_2 & a_1 & a_0 \\ 0 & b_3 & b_2 & b_1 & b_0 \end{vmatrix},$$

$$c_2 = \begin{vmatrix} 0 & 1 & x & 0 \\ 0 & 0 & 1 & x \\ a_3 & a_2 & a_1 & a_0 \\ b_3 & b_2 & b_1 & b_0 \end{vmatrix}, \quad c_1 = - \begin{vmatrix} 1 & x & 0 & 0 \\ 0 & 0 & 1 & x \\ a_3 & a_2 & a_1 & a_0 \\ b_3 & b_2 & b_1 & b_0 \end{vmatrix}, \quad c_0 = \begin{vmatrix} 1 & x & 0 & 0 \\ 0 & 1 & x & 0 \\ a_3 & a_2 & a_1 & a_0 \\ b_3 & b_2 & b_1 & b_0 \end{vmatrix}, \quad \gamma_2 = \begin{vmatrix} d_2 & d_1 \\ c_2 & c_1 \end{vmatrix}, \quad \gamma_3 = \begin{vmatrix} d_2 & d_0 \\ c_2 & c_0 \end{vmatrix},$$

$$\gamma_4 = \begin{vmatrix} d_1 & d_0 \\ c_1 & c_0 \end{vmatrix}, \quad \gamma_5 = \begin{vmatrix} d_2 & d_1 & d_0 \\ c_2 & c_1 & c_0 \\ 0 & d_2 & d_1 \end{vmatrix}, \quad \gamma_6 = \begin{vmatrix} d_2 & d_1 & d_0 \\ c_2 & c_1 & c_0 \\ 0 & c_2 & c_1 \end{vmatrix}, \quad \gamma_7 = \begin{vmatrix} d_1 & d_0 & 0 \\ d_2 & d_1 & d_0 \\ c_2 & c_1 & c_0 \end{vmatrix}, \quad \gamma_8 = \begin{vmatrix} c_1 & c_0 & 0 \\ d_2 & d_1 & d_0 \\ c_2 & c_1 & c_0 \end{vmatrix}$$

A minimal generating set

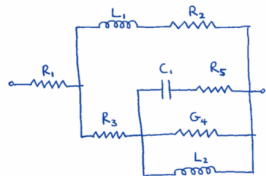

$$Z(s) = \frac{a(s)}{b(s)} = \frac{a_3 s^3 + a_2 s^2 + a_1 s + a_0}{b_3 s^3 + b_2 s^2 + b_1 s + b_0}$$

$$R_1 = \frac{\hat{a}}{\hat{b}}, \quad R_2 = \frac{\gamma_1 x}{\hat{b}^2}, \quad R_3 = \frac{\gamma_1 c_0}{\hat{b} d_0}, \quad G_4 = \frac{\hat{b} d_0 \gamma_7}{\gamma_4^2 \gamma_1},$$

$$R_5 = \frac{-\gamma_4^2 \gamma_3}{\hat{b}^3 d_0^2 S}, \quad L_1 = \frac{\gamma_1}{\hat{b}^2}, \quad L_2 = \frac{-\gamma_4 \gamma_1}{\hat{b} d_0^2}, \quad C_1 = \frac{-\hat{b}^3 d_0^2 S}{\gamma_4^3}$$

$\exists x \geq 0$ such that one of the following holds:

- (a) $\hat{b} > 0, \gamma_7 \geq 0, \gamma_1 > 0, S > 0, \hat{a} \geq 0, \gamma_4 < 0, \gamma_3 \leq 0, c_0 \leq 0, d_0 < 0;$
- (b) $\hat{b} > 0, \gamma_7 \leq 0, \gamma_1 > 0, S > 0, \hat{a} \geq 0, \gamma_4 < 0, \gamma_3 \leq 0, c_0 \geq 0, d_0 > 0;$
- (c) $\hat{b} < 0, \gamma_7 \geq 0, \gamma_1 > 0, S > 0, \hat{a} \leq 0, \gamma_4 > 0, \gamma_3 \geq 0, c_0 \leq 0, d_0 > 0;$
- (d) $\hat{b} < 0, \gamma_7 \leq 0, \gamma_1 > 0, S > 0, \hat{a} \leq 0, \gamma_4 > 0, \gamma_3 \geq 0, c_0 \geq 0, d_0 < 0;$

Show that if any one of conditions (a)–(d) hold, then x can be altered to make either $\hat{a} = 0, c_0 = 0, \gamma_7 = 0, \gamma_3 = 0$ or $x = 0$ (without violating any of the other inequalities)

Higher degree


Minimally reactive

Degree	Series-parallel	General
Bilinear	2 resistors	2 resistors
Biquadratic	3 resistors	3 resistors
Bicubic	4 resistors	
Degree n		

Higher degree

Minimally reactive



Degree	Series-parallel	General
Bilinear	2 resistors	2 resistors
Biquadratic	3 resistors	3 resistors
Bicubic	4 resistors	
Degree n	$2n - 1$ resistors	

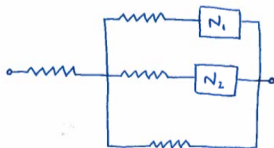

Higher degree

Minimally reactive

Degree	Series-parallel	General
Bilinear	2 resistors	2 resistors
Biquadratic	3 resistors	3 resistors
Bicubic	4 resistors	
Degree n	$2n - 1$ resistors	$(n + 1)(2n + 1)$ resistors

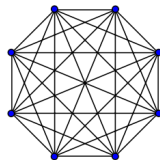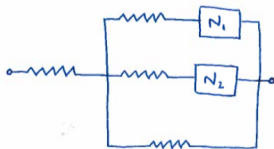

Note on mechanical design

- Considered problem of realising bicubic impedance with a series-parallel network containing 3 reactive elements (no limit on no. of resistors/dampers)
- Case of 3 inductors or 3 capacitors is known. Considered 2 inductors + 1 capacitor (case of 1 inductor + 2 capacitors is similar)
- Showed impedance is always realised by one of < 50 series-parallel networks, each containing 3 reactive elements and 4 resistors
- Realisability conditions of form: $\exists x \geq 0$ such that $f_1(x) = 0$, $f_2(x) \geq 0, \dots, f_m(x) > 0, \dots$
- Quantifier elimination can remove x , but not pretty!
- In practice: root finding algorithms give (approximate) realisations